


ELECTRIC DIYA



MATERIAL REQUIRED



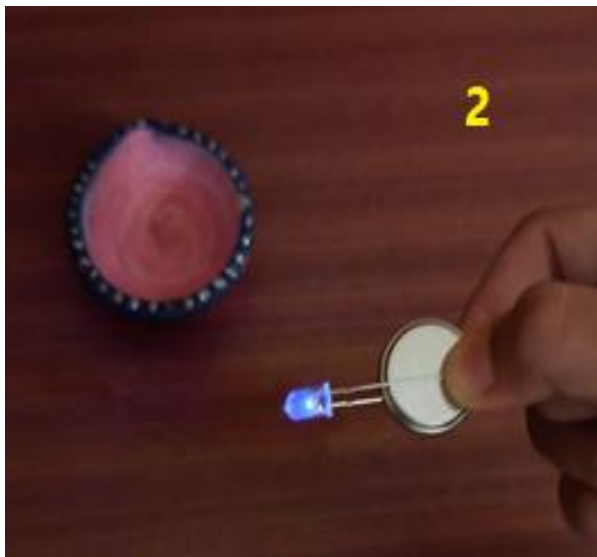FIX THE TERMINALS OF LED WITH THE CELL HELP OF INSULATIVE TAPE



ATTACH CELL WITH THE LED



ELECTRIC DIYA IS READY

ELECTRIC CIRCUIT OF LED WITH CELL IS COMPLETE AND IT STARTS GLOWING.

ARSHA SARAF'S LAB